

Topic 5

Single Cycle Processor

Introduction

- Starting from this topic, we will examine two RISC-V implementations
 - A simplified version
 - A more realistic pipelined version
- Supporting a simple subset, shows most aspects of RISC-V design
 - Memory reference: lw, sw
 - Arithmetic/logical: add, sub, and, or
 - Control transfer: beq
- You are expected to be able to change the hardware to support more instructions


Instruction Execution

- PC \rightarrow program memory, fetch instruction
- Use register addresses to access register file, read registers
- Depending on instructions
 - Use ALU/Adder to calculate
 - Arithmetic/logic result
 - Memory address for load/store
 - Branch target address
- Access register file or data memory for load or store or save calculation results
- Update PC \leftarrow target address or PC + 4

Building a Datapath


- Datapath
 - Elements that process, store, or route data in the CPU
 - E.g. registers, ALUs, mux's, memories, ...
- We will build a RISC-V datapath incrementally
- We will add a control unit to provide control signals to the datapath

Instruction Fetch

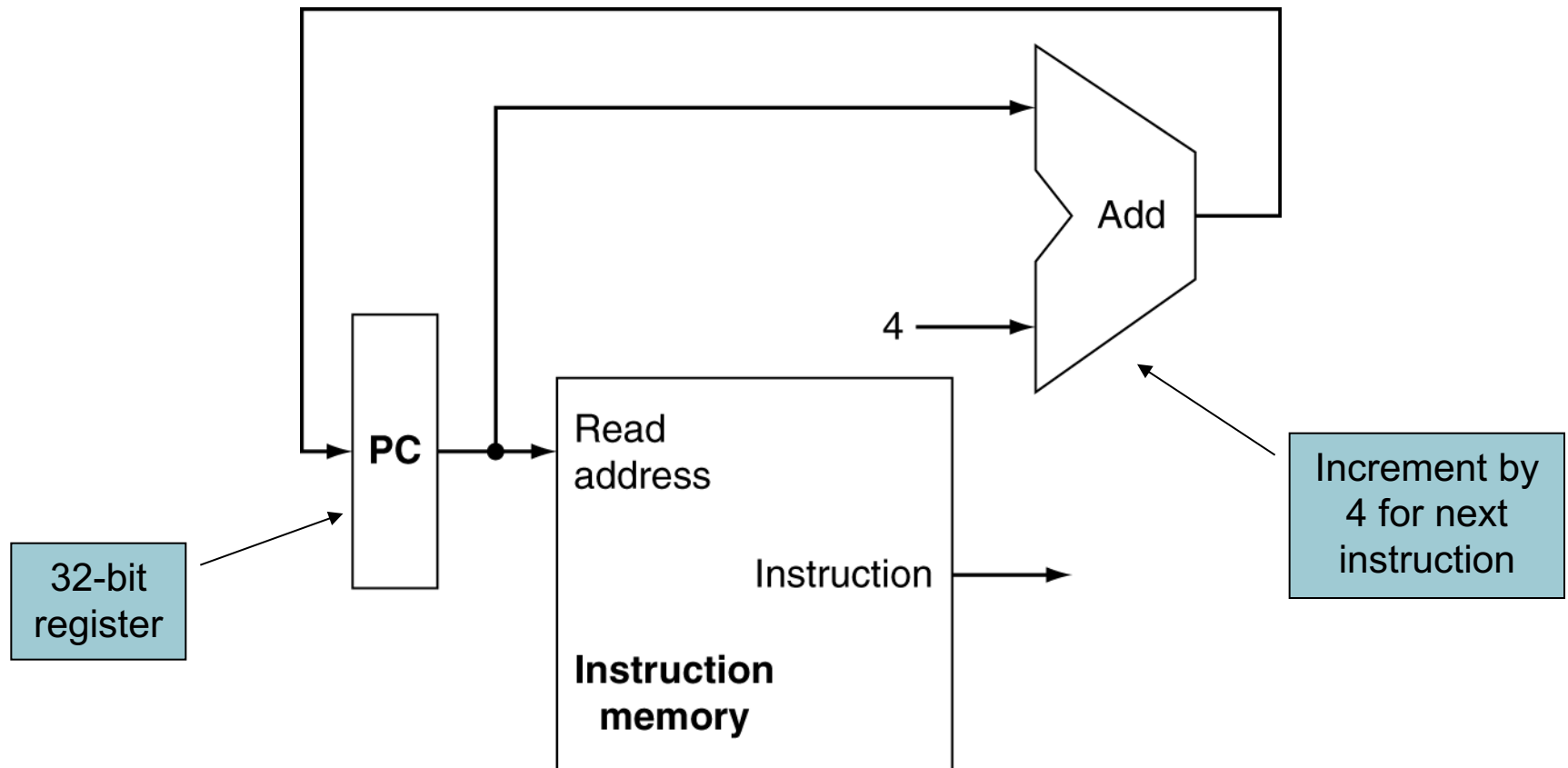


R-Format Instructions

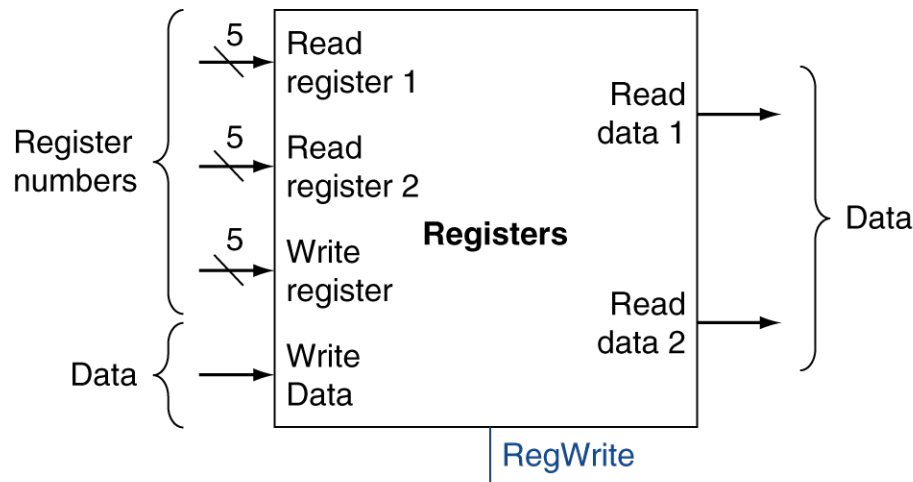- Operations:
 - Read two register operands
 - Perform arithmetic/logical operation
 - Write register result
- We need:




a. Registers

 

 
b. ALU

Load/Store Instructions

- Operations:
 - Read register operands
 - Calculate address using 12-bit immediate
 - Load: Read memory and update register
 - Store: Write register value to memory
- Additionally, we need:



a. Data memory unit

 

b. Immediate generation unit

Beq Instructions

- Operations:

- Read register operands

- Compare operands

- $rs1 == rs2? \rightarrow rs1 - rs2 == 0?$

- Use ALU, subtract then check the Zero output of the ALU

- Calculate target address

Target PC = Current PC + immediate \times 2


- Sign-extend the immediate

- Shift left 1 place (multiply by 2)

- Add to PC value

Branch Instructions

- We need:

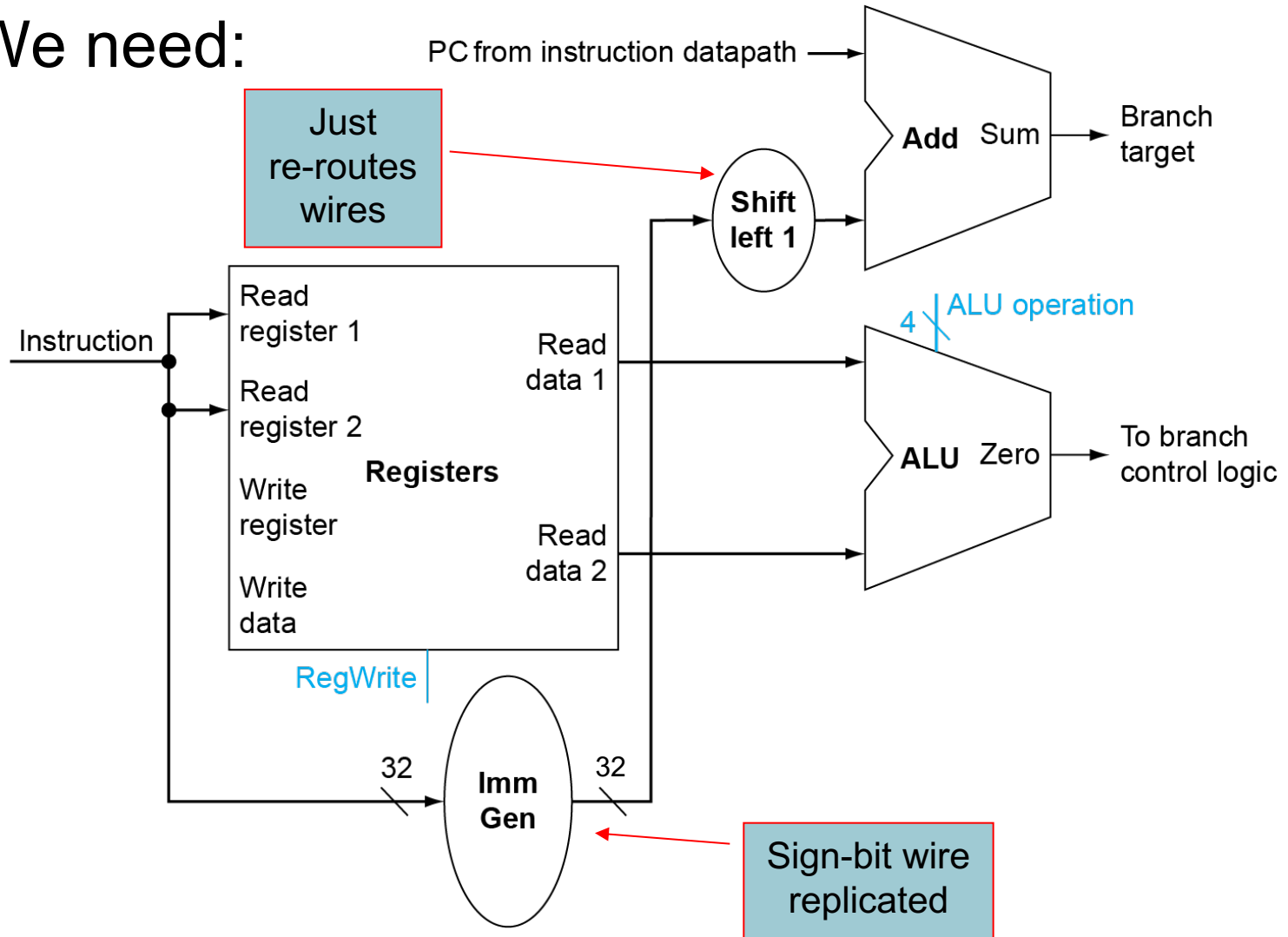

Performance Considerations


Type	Field					
	7 bits	5 bits	5 bits	3 bits	5 bits	7 bits
I-type	immediate[11:0]		rs1	funct3	rd	opcode
S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode
B-type	immed[11,9:4]	rs2	rs1	funct3	immed[3:0,10]	opcode
U-type	immediate[19:0]				rd	opcode
J-type	immediate[19,9:0,10,18:11]				rd	opcode

- In B-type (SB-type) and J-type (UJ-type), immediate bits are swirled around
 - It saves hardware (muxes) in “**Imm Gen**” component which picks different fields in an instruction to assemble the immediate number according to different type of the instruction

Composing the Elements


- First version of datapath execute an instruction in one clock cycle
 - Each datapath element can only do one function at a time
 - Hence, we need separate instruction memory and data memory
- Use multiplexers where alternate data sources are used for different instructions

Combine The Operations

 


Add Multiplexers

 
- Can't just join wires together
 - Use multiplexers



Add Control Singals

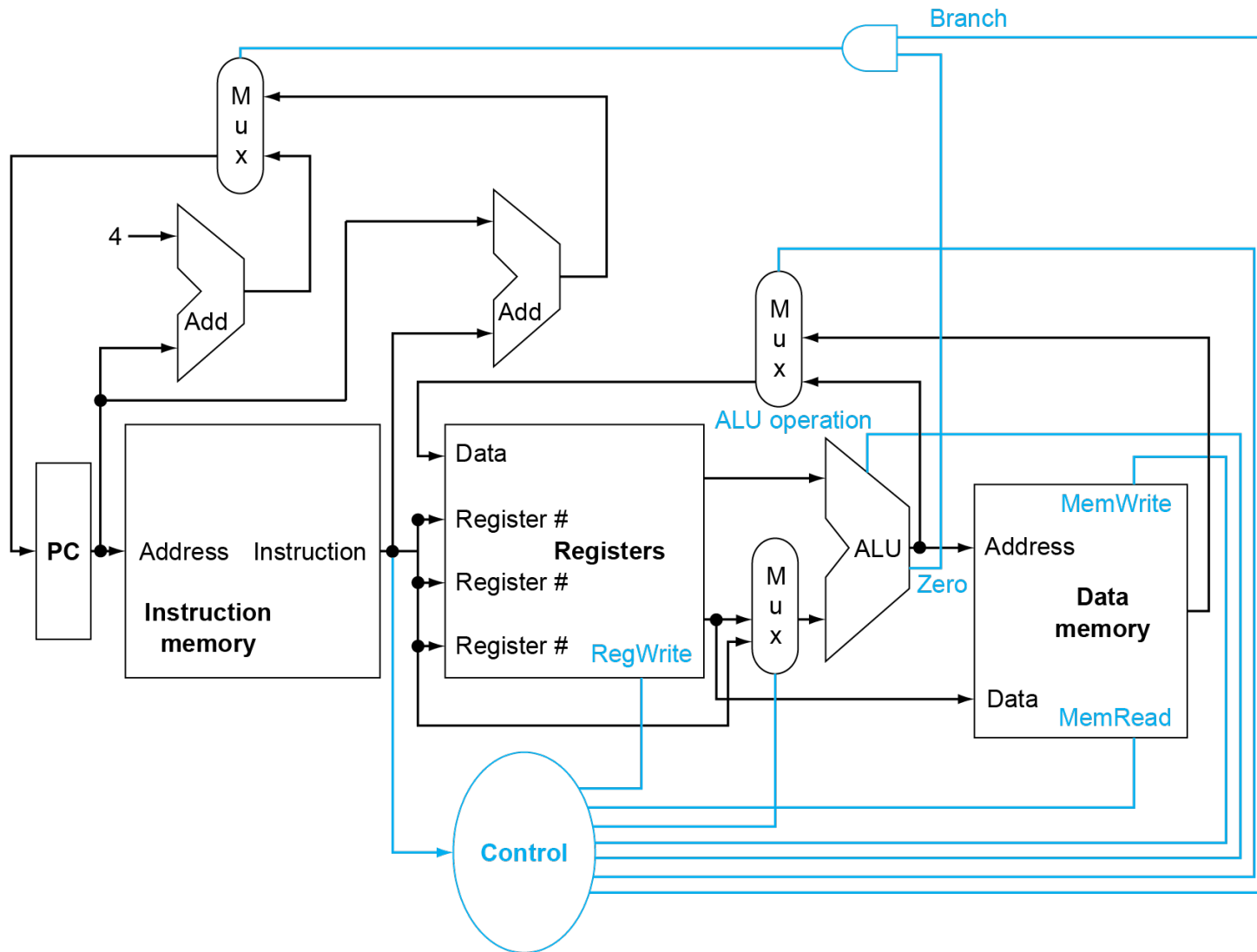


Putting Everything Together

 


Performance Consideration

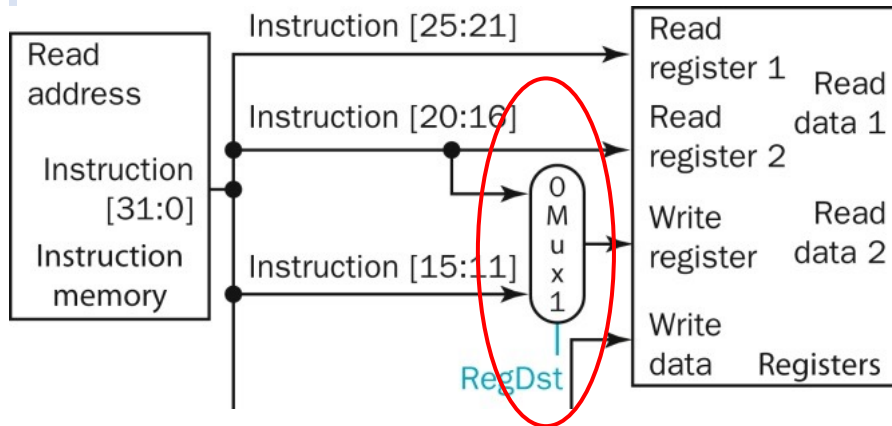- RISC-V has more types (6) than MIPS (4)
 - But it saves hardware on the critical path



MIPS Architecture: simpler instruction format, but more complicated hardware, longer delay

V.S.

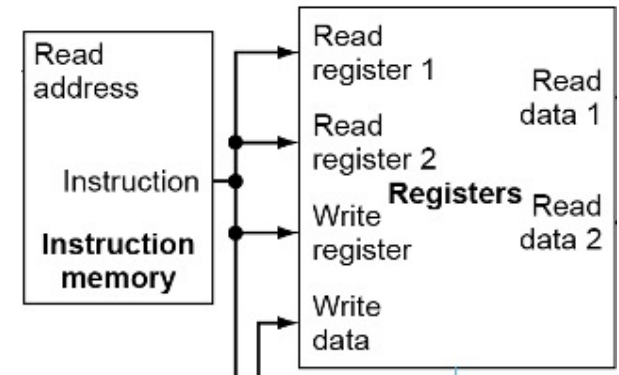

RISC-V Architecture: more complicated instruction format, but simpler hardware, thus better performance


Add ALU Control

- ALU used for
 - Load/Store: Function = add
 - Branch: Function = subtract
 - R-type: Function depends on opcode

ALU control Signal	Function
0000	AND
0001	OR
0010	add
0110	subtract


ALU Control Unit

 - ALU Control is a combinational logic
 - Assume 2-bit ALUOp derived from opcode




Instr.	Operation	ALU function	Opcode field	ALUOp (input)	i[30] (input)	funct3 (input)	ALU control (output)
lw	load register	add	XXXXXXXX	00	X	010	0010
sw	store register	add	XXXXXXXX	00	X	010	0010
beq	branch on equal	subtract	XXXXXXXX	01	X	000	0110
R-type	add	add	100000	10	0	000	0010
	subtract	subtract	100010		1	000	0110
	AND	AND	100100		0	111	0000
	OR	OR	100101		0	110	0001


Datapath With Control Unit

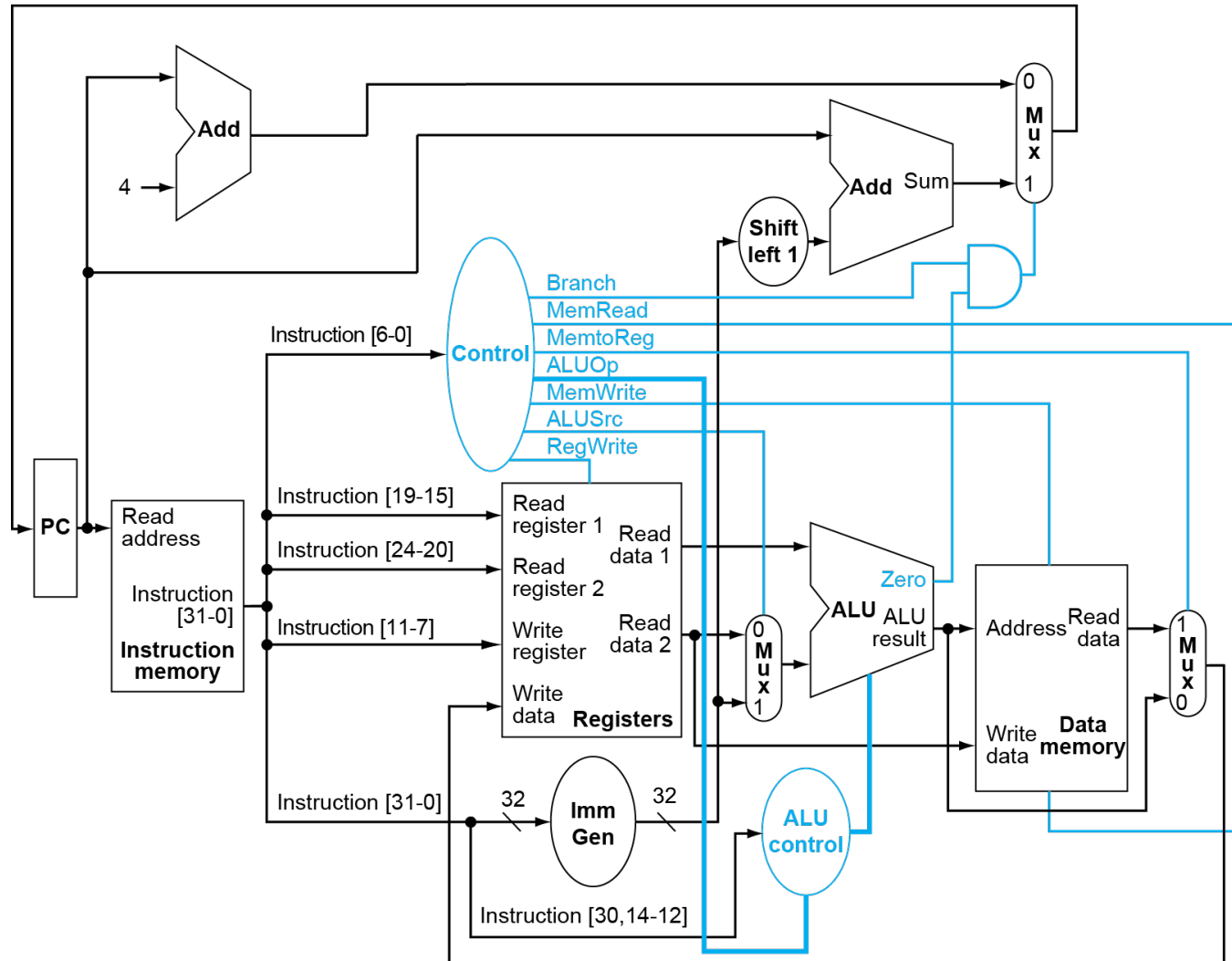


R-Type Instruction

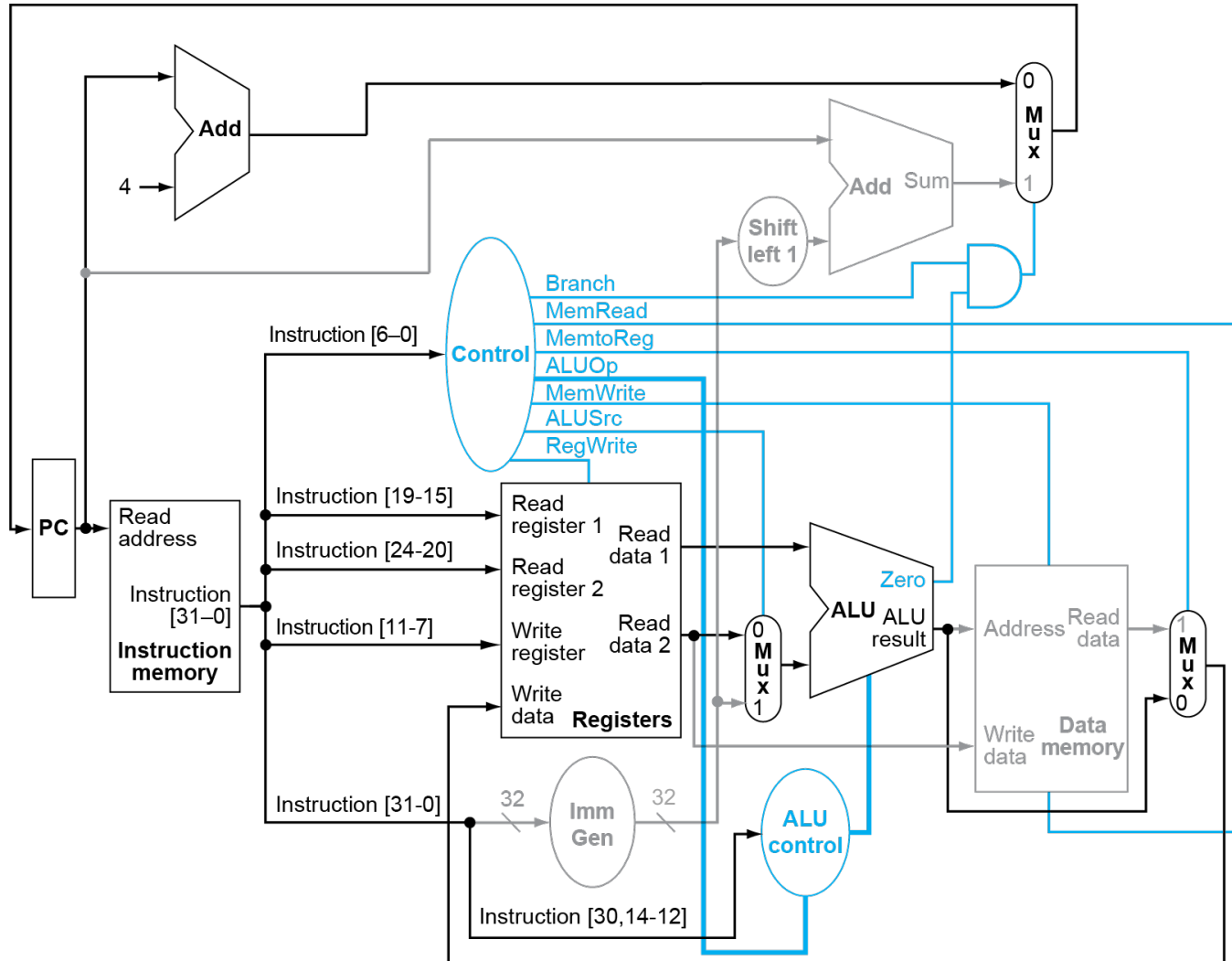

Load Instruction

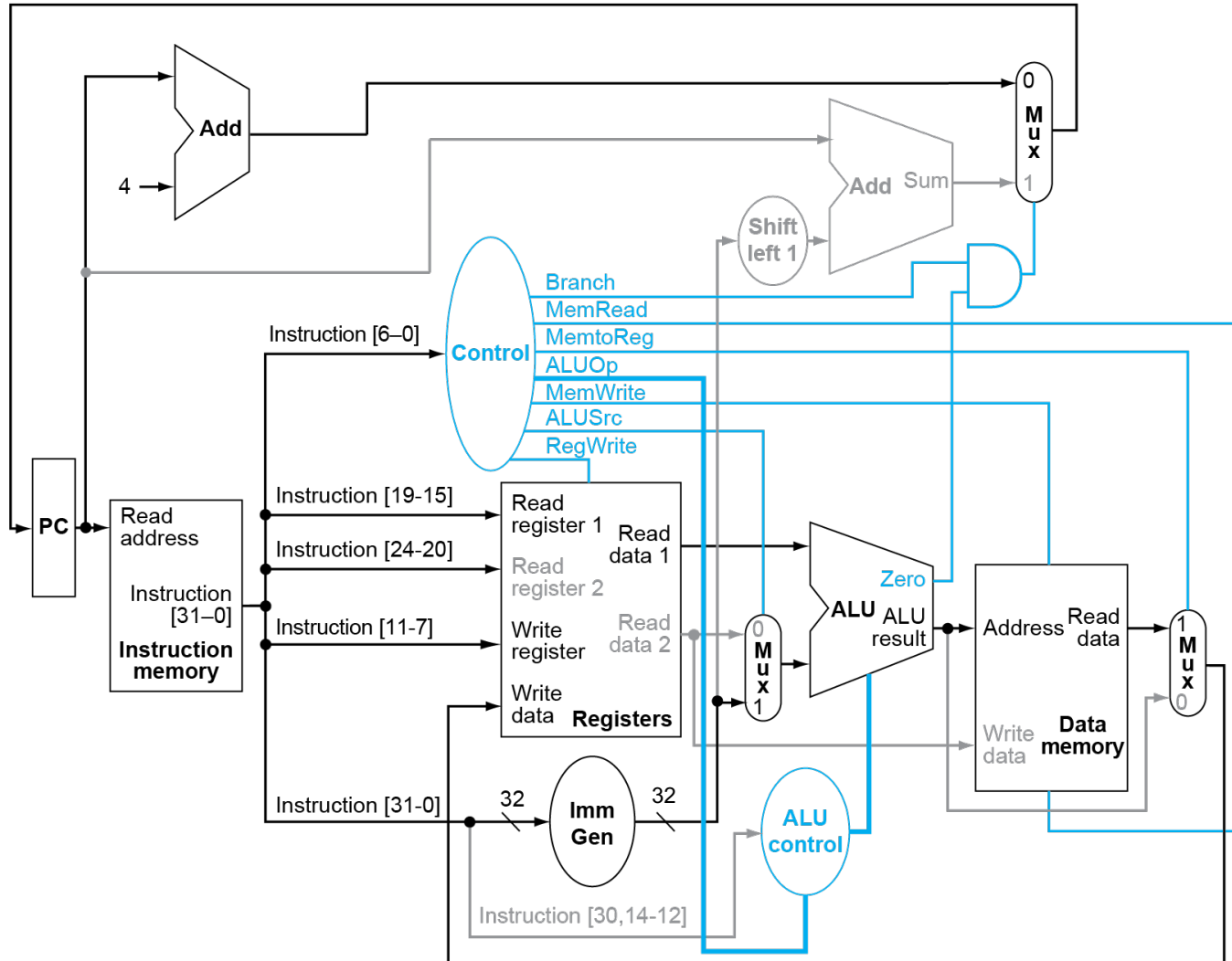

Branch-on-Equal Instruction

 

Control Signals

- Control signals derived from instruction

Inst.	ALU Src	Reg Dst	ALU Op	Mem Write	Mem Read	Branch	Memto Reg	Reg Write
add								
addi								
lw								
sw								
beq								

Performance Related Factors

- Algorithm
 - Determines number of operations executed
- Programming language, compiler, architecture
 - Determine number of machine instructions (lines of source code) executed per operation
- Processor and memory system
 - Determine how fast instructions are executed
- I/O system (including OS)
 - Determines how fast I/O operations are executed

How to Measure Computer Performance?

- Execution (response) time
 - How long it takes to do a task
 - Measure for PCs and embedded computers
- Throughput
 - Total work done per unit time
 - Servers


We'll focus on **execution time** for now

Execution Time

- Elapsed time – for System Performance
 - Total execution time to complete a task, including
 - Processing, I/O, OS overhead, idle time, everything
 - But doesn't completely reflect computer's performance if it focuses on better throughput
- CPU time – for CPU Performance
 - CPU execution time processing a task
 - Exclude I/O time, time spent for other tasks
 - Comprises **user CPU time** and **system CPU time**
 - Hard to differentiate
 - Different programs run with different CPU performance and system performance

CPU Clocking

 - Operation of digital hardware governed by a constant-rate clock



- Clock period: duration of a clock cycle
 - e.g., $250\text{ps} = 0.25\text{ns} = 250 \times 10^{-12}\text{s}$
- Clock frequency (rate): cycles per second
 - e.g., $4.0\text{GHz} = 4000\text{MHz} = 4.0 \times 10^9\text{Hz}$

CPU Time

$$\begin{aligned}\text{CPU Time} &= \text{CPU Clock Cycles} \times \text{Clock Cycle Time} \\ &= \frac{\text{CPU Clock Cycles}}{\text{Clock Rate}}\end{aligned}$$

- Performance improved by
 - Reducing number of clock cycles
 - Increasing clock rate
 - Hardware designer must often trade off clock rate against cycle count

CPU Time Example

- Computer A: 2GHz clock, 10s CPU time
- Designing Computer B
 - Aim for 6s CPU time
 - Can do faster clock, but causes $1.2 \times$ clock cycles
- How fast must Computer B clock be?

$$\text{Clock Rate}_B = \frac{\text{Clock Cycles}_B}{\text{CPU Time}_B} = \frac{1.2 \times \text{Clock Cycles}_A}{6s}$$

$$\begin{aligned}\text{Clock Cycles}_A &= \text{CPU Time}_A \times \text{Clock Rate}_A \\ &= 10s \times 2\text{GHz} = 20 \times 10^9\end{aligned}$$

$$\text{Clock Rate}_B = \frac{1.2 \times 20 \times 10^9}{6s} = \frac{24 \times 10^9}{6s} = 4\text{GHz}$$

Instruction Count and CPI

Clock Cycles = Instruction Count \times Cycles per Instruction

CPU Time = Instruction Count \times CPI \times Clock Cycle Time

$$= \frac{\text{Instruction Count} \times \text{CPI}}{\text{Clock Rate}}$$

- Instruction Count (IC) for a program
 - Determined by program, ISA and compiler
- Average cycles per instruction (CPI)
 - Determined by CPU hardware
 - If different instructions have different CPI
 - Average CPI affected by instruction mix

CPI Example

- Computer A: Cycle Time = 250ps, CPI = 2.0
- Computer B: Cycle Time = 500ps, CPI = 1.2
- Same ISA
- Which is faster, and by how much?

$$\begin{aligned}\text{CPU Time}_A &= \text{Instruction Count} \times \text{CPI}_A \times \text{Cycle Time}_A \\ &= 1 \times 2.0 \times 250\text{ps} = 1 \times 500\text{ps} \leftarrow \text{A is faster...}\end{aligned}$$

$$\begin{aligned}\text{CPU Time}_B &= \text{Instruction Count} \times \text{CPI}_B \times \text{Cycle Time}_B \\ &= 1 \times 1.2 \times 500\text{ps} = 1 \times 600\text{ps}\end{aligned}$$

$$\frac{\text{CPU Time}_B}{\text{CPU Time}_A} = \frac{1 \times 600\text{ps}}{1 \times 500\text{ps}} = 1.2 \leftarrow \text{...by this much}$$

Performance Summary

The BIG Picture

$$\text{CPU Time} = \frac{\text{Instructions}}{\text{Program}} \times \frac{\text{Clock cycles}}{\text{Instruction}} \times \frac{\text{Seconds}}{\text{Clock cycle}}$$



- Performance depends on

- Algorithm: affects IC, possibly CPI
- Programming language: affects IC, CPI
- Compiler: affects IC, CPI
- Instruction set architecture: affects IC, CPI, T_c

Clock Period

Clocking Methodology

  - Combinational logic does the computation during clock cycles
 - Between clock edges
 - Input (present state) from state elements, output (next state) to state element
 - Among all kinds of computations, longest delay determines clock period



Performance Consideration

- Longest instruction determines the clock cycle time
 - Critical path: the path having longest delay
 - load instruction
Instruction memory → register file → ALU → data memory → register file (plus MUXes)
- Not feasible to vary period for different instructions
 - Waste time on other instructions
- How to improve the performance (faster speed)?